

Sl. No.

No. of Printed Pages : 2



**21BSC2C2ELL**

**B.Sc. II Semester (NEP) Degree Examination, September/October - 2022**

**ELECTRONICS**  
**Electronic Circuits**

Time : 3 Hours

Maximum Marks : 60

**Note :** Answer **all** Sections.

**SECTION - A**

1. Answer the following questions. **10x1=10**
- (a) What is power supply ?
  - (b) What is filter ?
  - (c) Define operating point.
  - (d) Define Stability factor.
  - (e) What is Amplification ?
  - (f) What is Cascaded Stage ?
  - (g) What is decibel ?
  - (h) What is ripple factor ?
  - (i) What is regenerative feedback ?
  - (j) What is monolithic IC regulator ?

**SECTION - B**

Answer **any four** : **4x5=20**

- 2. With neat circuit diagram explain the zener diode voltage regulator.
- 3. Explain Base resistor method transistor biasing.
- 4. Classification of amplifiers on the basis of parameters.
- 5. What is Darlington pair transistor ? Explain it.
- 6. With neat block diagram explain transistor audio power amplifier.
- 7. Define positive and negative feedback amplifier and merits of it.



**P.T.O.**

**SECTION - C**Answer **any three**.**3x10=30**

- 8.** Explain the working of centre tapped Full Wave rectifier. Obtain the expressions for the efficiency.
- 9.** Explain the working of emitter-feedback biasing network and obtain different expressions.
- 10.** Explain the working of transformer coupled amplifier and discuss the frequency response.
- 11.** Explain the working of Class-B push-pull amplifier obtain the expression for the power efficiency.
- 12.** Define the expression for the voltage gain of the negative feedback amplifier. Mention its merits.
- 13.** Write a short note on :
  - (a) 78 XX Series regulators
  - (b) Hybrid parameters

**- o O o -**