

## M.Sc. I Semester Degree Examination, April/May - 2024

### PHYSICS

### Electronics

### (NEP)

Time : 3 Hours

Maximum Marks : 70

**Note :** Answer **any five** of the following questions with Question No. **1 (Q.1)** is **Compulsory**.  
Each question carries **equal** marks.

1. (a) What is carrier concentration ? Derive the expression for carrier concentration in an n-type semiconductor. **9**  
(b) What is the Fermi level ? Explain its variation with temperature in semiconductors. **5**
2. (a) Describe the operation of a transistor in a common emitter (CE) configuration. **8**  
(b) Describe how feedback criteria in electronic circuits contribute to sustained oscillations. **6**
3. (a) How does an op-amp integrator circuit operate ? Explain how it performs mathematical integration of the input signal. **7**  
(b) Discuss the principles and operation of active filters. What are the characteristics of first-order filter functions ? **7**
4. (a) What are Boolean operations and how are they used in digital electronics ? **8**  
(b) What is a Karnaugh map and how is it used to simplify Boolean expressions ? **6**
5. (a) Explain the operation of an RS flip-flop. How does it differ from other types of flip-flops like D and JK flip-flops ? **8**  
(b) Calculate the output of a binary ripple counter with four bits, starting from the initial state 0000 and incrementing with each clock pulse. **6**
6. (a) Discuss the operational characteristics of a MOSFET in common drain (CD) configuration. **7**  
(b) Explain the basic principles behind the operation of a phase-shift oscillator. **7**

7. (a) Explain the difference between product of sums (POS) and sum of products (SOP) simplification techniques with an example. **7**
- (b) Compare and contrast the characteristics of binary weighted and R-2R ladder digital-to-analog converters (DACs). **7**
8. (a) Calculate the voltage across a Si diode at room temperature, if it is forward biased with a current of 10 mA. Assume a typical barrier potential of 0.7 volts. **5**
- (b) Calculate the base current ( $I_B$ ) of a bipolar junction transistor (BJT) operating in a CE configuration if the collector current ( $I_C$ ) is 2 mA and the current gain ( $\beta$ ) is 100. **5**
- (c) If an A/D converter has a resolution of 8 bits, what is the maximum number of discrete levels it can represent ? **4**

- o 0 o -

