



B.Sc. I Semester Degree Examination, April/May - 2024

ELECTRONICS
DSC 1 : Basic Electronics
(NEP)

Time : 2 Hours

Maximum Marks : 60

Note : Answer **all** sections.

SECTION - A

1. Answer the following sub-questions. **10x1=10**
- (a) Define passive components.
 - (b) What is the unit of capacitance ?
 - (c) What is phase in A.C circuits ?
 - (d) Define Network and Junction.
 - (e) What is Valence electron ?
 - (f) What is knee voltage ?
 - (g) Expand the term LED.
 - (h) What is transistor ?
 - (i) Define Donor in semiconductor.
 - (j) Expand JFET.

SECTION - B

- Answer **any Four** questions. **4x5=20**
2. What is fixed Resistors ? Explain in brief.
3. Explain the following terms :
- (i) Amplitude
 - (ii) Time period
 - (iii) Voltage
 - (iv) Peak factor
 - (v) Complex number
4. State KCL and KVL in network theorems.
5. Explain the working of P-type semiconductor.
6. Explain the construction and working of LED and write applications.
7. Explain the working principle of PNP transistor.



SECTION - C

Answer **any Three** questions.

3x10=30

8. Explain the construction of carbon composition color code resistor with color code chart.
9. Derive the expression for RMS value of a sinusoidal wave form.
10. State and prove maximum power transformer theorem.
11. With neat circuit diagram explain Pn junction diode in forward and reverse bias and draw V-I characteristics curve.
12. Explain the CB, CE and CC configurations of transistors.

- o O o -

